## Digital Stopwatch

Submitted by

Neha Sethumadhavan (20323080) Roopesh O R (20323085) Roshna Palatty Santhosh (20323086) Sreenandan C K (20323096) Merella Jobi (LET B2)



Division of Electronics Engineering
School of Engineering
Cochin University of Science and Technology
Kochi - 682022

September 2024

## Abstract

Here we present the design and implementation of a digital stopwatch using a 555 timer as the clock source. The stopwatch displays time in minutes and seconds, utilizing basic digital electronics components such as counters, decoders, and seven-segment displays. The 555 timer is configured in astable mode to generate a clock pulse with a frequency of 1 Hz, serving as the time base for the stopwatch. A series of 60-second counts is accumulated for the seconds, and upon reaching 60, a minute counter increments. These counters are implemented using combination of binary and decade counters, and the output is decoded and displayed on four seven-segment displays, two for minutes and the other two for seconds. Control functionalities include start, stop, and reset buttons are also present to control the operation of the stopwatch.

## **Project Estimate**

| Components               | Quantity | Approx. Cost |
|--------------------------|----------|--------------|
| 7447 - 7 segment decoder | 4        | 80           |
| 7408 - AND gate          | 2        | 20           |
| 7432 - OR gate           | 2        | 20           |
| 7404 - NOT gates         | 1        | 15           |
| 7490 - decade counter    | 2        | 70           |
| 7493 - 4bit counter      | 2        | 70           |
| 555 timer                | 1        | 15           |
| Breadboard               | 4-5      | $\sim 200$   |
| Capacitor                | 4-5      | $\sim 20$    |
| Resistors                | 35       | $\sim 40$    |
| 7 segment display        | 4        | 120          |
| Potentiometer (100k)     | 1        | 20           |
| Total                    |          | $\sim 690$   |